



# Rajiv Gandhi Institute of Petroleum Technology

## Department of Electronics Engineering

**Subject:** Electronics Engineering Work Practices

**Maximum Marks:** 30

Note: All questions are compulsory. Be precise while answering the questions.

**Pb.1.** Draw the circuit diagram of AC to regulated DC power converter where, the input will be 230 V AC and output should be 9V DC. What are the components (with values) employ here, define? Show the waveform at each and every step of the circuit. .... 5 Marks

**Pb.2.** For the network shown in figure 1. .... 5 Marks

a. Determine the range of  $R_L$  and  $I_L$  that will result in  $V_{RL}$  being maintained at 10 V.

b. Determine the maximum wattage ranging of Zener Diode.

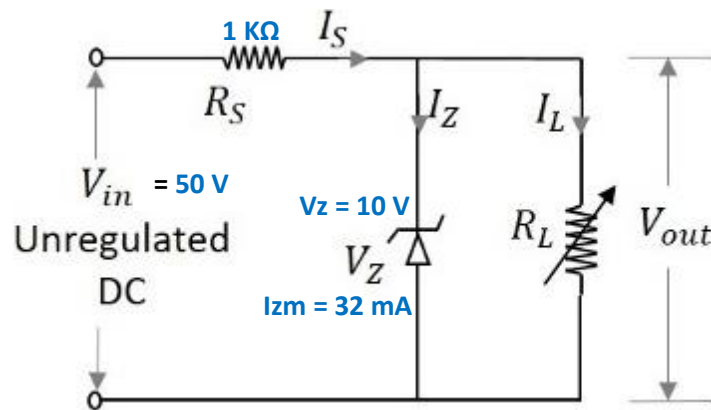


Figure 1

**Pb.3.** Determine  $V_o$  waveform for the network shown in Figure 2. Treat diode as an Ideal diode. .... 5 Marks

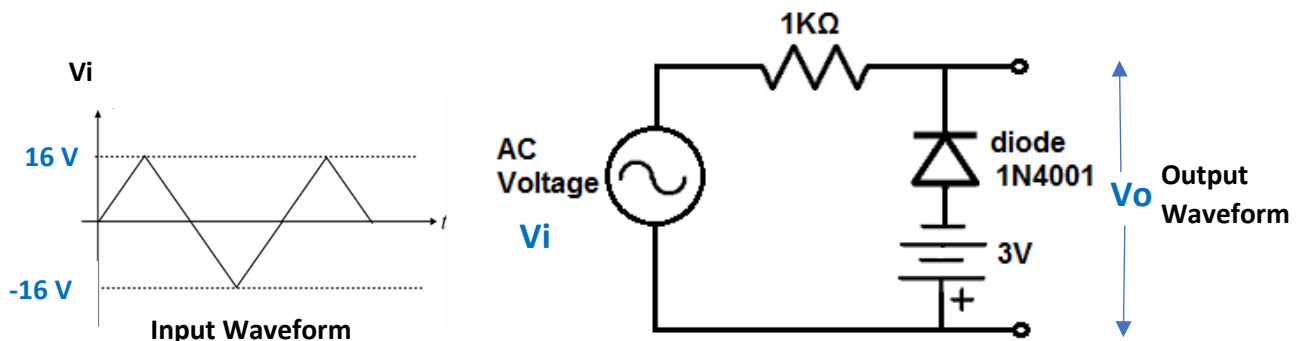


Figure 2

**Pb.4.** Describe the charging and discharging phenomena of parallel plate capacitor. What is the relation between capacitance and parallel plate area? .... 4 Marks

**Pb.5.** There are some multiple-choice questions. Only one option is correct. Each question has equal marks. .... **6 Marks**

- a.** An ideal ammeter has ..... resistance
1. Low
  2. Infinite
  3. Zero
  4. High
- b.** A voltmeter should have ..... resistance
1. Zero
  2. Very high
  3. Very low
  4. None of the above
- c.** Two multimeters A and B have sensitivities of 10 k $\Omega$ /V and 30 k $\Omega$ /V respectively. Then .....
1. Multimeter A is more sensitive
  2. Multimeter B is more sensitive
  3. Both are equally sensitive
  4. None of the above
- d.** What do you mean by 4 and  $\frac{1}{2}$  display?
1. Four digits will display 0 to 9 and one digit which is at MSB (most significant bit) will display 0 or 1.
  2. Four digits will display 0 to 9 and one digit which is at LSB (least significant bit) will display 0 or 1.
  3. Four digits will display 0 to 1 and one digit which is at MSB (most significant bit) will display 0 or 9.
  4. Four digits will display 0 to 1 and one digit which is at LSB (most significant bit) will display 0 or 9.
- e.** There are four capacitors ( $C_1$ ,  $C_2$ ,  $C_3$ , and  $C_4$ ) connected in series. What is the value of overall capacitance?
1.  $C_T = C_1 + C_2 + C_3 + C_4$
  2.  $C_T = 1/((1/C_1) + (1/C_2) + (1/C_3) + (1/C_4))$
  3.  $C_T = (1/C_1) + (1/C_2) + (1/C_3) + (1/C_4)$
  4.  $C_T = 1/(C_1 + C_2 + C_3 + C_4)$
- f.** Maximum allowable current for any resistance setting is calculated as:
1.  $I_{max} = \sqrt{P/R}$ , Where P = Power and R = Resistance
  2.  $I_{max} = 1/\sqrt{PxR}$ , Where P = Power and R = Resistance
  3.  $I_{max} = \sqrt{R/P}$ , Where P = Power and R = Resistance
  4.  $I_{max} = 1/\sqrt{P/R}$ , Where P = Power and R = Resistance

**Pb.6.** Define PN Junction Diode. Draw its V-I characteristics and define its equivalent circuit.

..... **5 Marks**